

# TAKAAB – Odd Clock Divider

---

- [Manual PDF](#)

---

[TAKAAB OCD - Odd Clock Divider – Siam Modular Manual PDF](#)

---

## Creative Applications for the TAKAAB OCD Odd Clock Divider

---

The TAKAAB OCD is a 2HP Eurorack clock divider focusing on *odd* and less common rhythmic divisions (1/3, 1/5, 1/7, 1/9 or optionally 1/6, 1/10). This unique approach opens the door to highly creative clocking, rhythmic, and generative possibilities in a modular synth environment.

Below are several creative uses for the OCD module, along with suggestions for modules you can pair it with:

---

### 1. Polyrhythmic Sequencing

---

#### How:

Divide a master clock into non-standard ratios (e.g., 1/3, 1/5, 1/7...) and use each output to advance different sequencers, drum modules, or envelope generators.

**Module Pairings:** - **Sequencers:** (e.g., Make Noise Rene, Intellijel Metropolis, or any analog step sequencer) - **Triggerable Drums:** (e.g., Mutable Instruments Peaks, Tiptop Audio ONE, or Erica Synths Drum Series modules) - **Envelope Generators:** (e.g., Maths, Intellijel Quadra)

### **Result:**

You'll achieve polyrhythmic patterns, constantly shifting relationships between parts, and evolving generative melodies or beats.

---

## **2. Rhythmic Modulation**

---

### **How:**

Send various odd-division clocks into modulation destinations for asynchronous rhythmic movement—like modulating a filter cutoff, LFO reset, or sample-and-hold.

**Module Pairings:** - **VCF/VCA modules:** Modulate or open a VCA only every 5th or 7th clock pulse. - **S&H or Slew Generators:** Trigger a S&H (like Mutable Kinks, Doepfer A-148) with 1/7 for unpredictable but repeating modulation steps.

### **Result:**

Create organic, evolving modulation where movement never quite repeats in sync.

---

## **3. Clocked Logic and Boolean Rhythms**

---

### **How:**

Combine the odd-divided outputs using logic modules for unexpected rhythmic interplay.

**Module Pairings:** - **Logic Modules:** (e.g., Takaab 2XOR, Mutable Instruments Kinks, Intellijel Plog) - **Other Clock Dividers/Multipliers:** Cascade even/odd dividers for dense rhythmic textures.

### **Result:**

Use AND, OR, XOR, etc., between divisions (e.g., 1/3 and 1/5) to produce even more complex and less predictable rhythmic triggers.

---

## 4. Self-Resetting Clock Chaos

---

### How:

Patch an OCD divided output (e.g., 1/5) back into the OCD's RESET input or into another OCD/ECD's reset, for cyclical yet phase-shifting rhythm resets.

**Module Pairings:** - **Chained Dividers:** Use the header connections or patch

cable for OCD/ERC daisy-chaining (jumpers/cables included). - **Logic for**

**Resequencing:** Logic modules can consolidate/reset multiple rhythmic divisions simultaneously.

### Result:

Shifting, non-traditional loop lengths and evolving cycles—perfect for generative, non-repetitive music.

---

## 5. Asynchronous Drum and Percussion Patterns

---

### How:

Trigger drum voices with the odd division outputs (1/3, 1/5, etc.) independently from "on-the-grid" main drums.

**Module Pairings:** - **Modular Drum Modules:** Tiptop Audio (BD808, SD808, etc.), Noise Engineering Basimilus Iteritas, ALM Akemie's Taiko. - **Sample**

**Players:** Trigger sample start with an odd division for shifting "offbeat" fills.

### Result:

Unconventional drum fills, evolving breaks, or percussion patterns that feel "alive" due to their refusal to lock to 4/4 time.

---

## 6. Generative Melodic Sequencing

---

### How:

Step a quantizer or precision adder (e.g., Doepfer A-156, Intellijel Scales)

with an odd divider, while other sequencers run at standard or different divisions.

**Result:**

Melodies that interact with other parts in semi-random but ultimately predictable long cycles, creating generative melody/chord relationships.

---

## 7. Clock-Based Probability and Randomization

---

**How:**

Trigger random modules (e.g., Mutable Marbles, Wobblebug) at odd divisions for irregular bursts of randomness.

**Result:**

Shifting, off-grid random gates or CVs for unpredictable but automatically cycling patterns.

---

### Bonus: Integrator with the Takaab ECD

**How:**

Pair the OCD with the Takaab ECD (Even Clock Divider) using the daisy-chain headers and reset/cascade features. Mix both even and odd divisions for comprehensive rhythm generation.

---

## Additional Tips

---

- The jumper to swap 1/9 for 1/6 is powerful for shifting patterns; consider bringing this function to your panel with the Takaab UXS.
- The outputs are 6V with a 50% duty cycle, so they work well with any typical Eurorack module expecting standard triggers/gates.
- Use in combination with clock delay or clock-multiplier modules for further rhythmic possibilities.

---

For more clock and logic patch ideas, visit the [Generated With Eurorack Processor](#) repository.